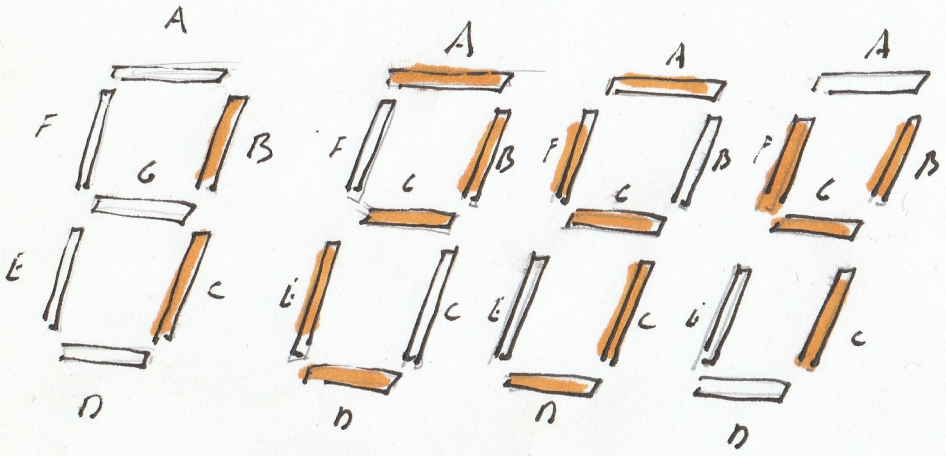

4 DIGIT 7 SEGMENT CLOCK

TIME 12:54

FIRST DOUBLE HOUR DIGIT B+C

SECOND SINGLE HOUR DIGIT A+B+D+E+G

DOUBLE MINUTE DIGIT A+C+D+F+G

SINGLE MINUTE DIGIT B+C+F+G

APPLIES TO LED AND PANAPLEX NEON

NEEDS 7x4 = 28 MICRO SWITCHES

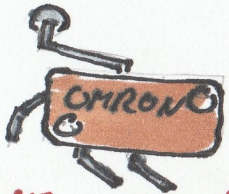

EACH DIGIT HAS (7) MICRO SWITCHES

SEVEN

4 DIGIT NIXIE CLOCK

12 54

FIRST DOUBLE HR DIGIT — CONNECT TO 1

SECOND SINGLE HOUR DIGIT — CONNECT TO 2

DOUBLE MINUTE DIGIT - CONNECT TO 5

SINGLE MINUTE DIGIT - CONNECT TO 4

APPLIES TO NIXIE NEON

NEEDS 29 MICRO SWITCHES FOR A 24 HR CLOCK WITH LEADING (0) IN DOUBLE HOUR DIGIT OR 27 MICRO SWITCHES FOR A 12 HOUR CLOCK WITH NO LEADING (0) ZERO

TO PREVENT CATHODE POISONING A LEADING ZERO ISN'T RECOMMENDED

12 HR CLOCK APPROPRIATE FOR MIXIE
24 HR CLOCK APPROPRIATE FOR LED OR PANAPLEX
5MM
4x10MM
40MM
4x 40 + 10 = 290 MM
300 TO 310 MM
INCLUDING PERFORATIONS
FOR SPROCKETS. ALIVE
ANY TO 35 MM FILM
ALIVE
12 59
12 58
12 57
12 56
12 55
12 54
12 59
12 58
12 57
12 56
12 55
12 54

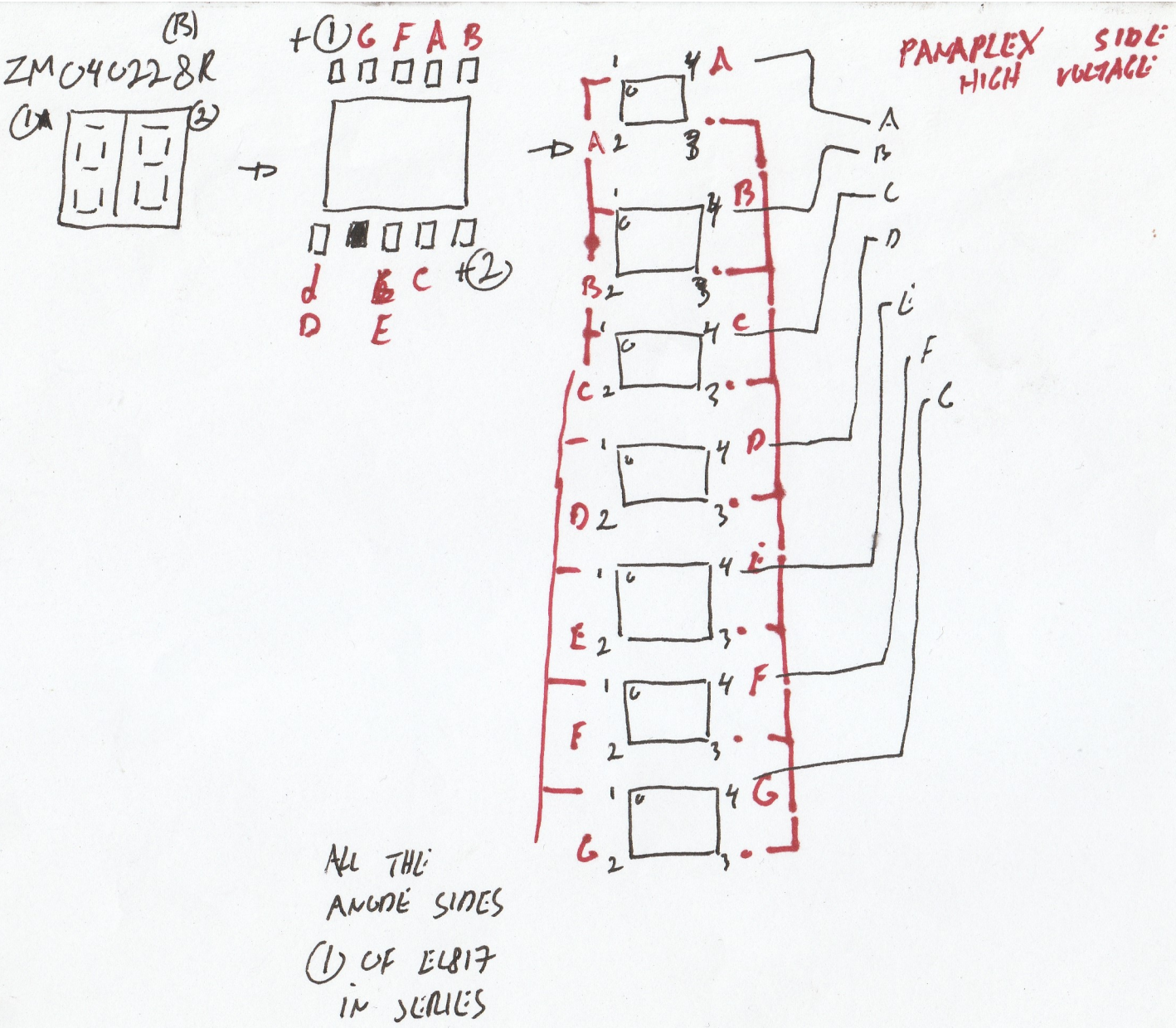
ZM040228R
(B)
(1A)
(2)
+(1) G F A B
d D
b E
C
+(2)
PAMAPLEX HIGH VOLTAGE SIDE
A
B
C
D
E
F
G
ALL THE ANODE SIDES
(1) OF EL817 IN SERIES

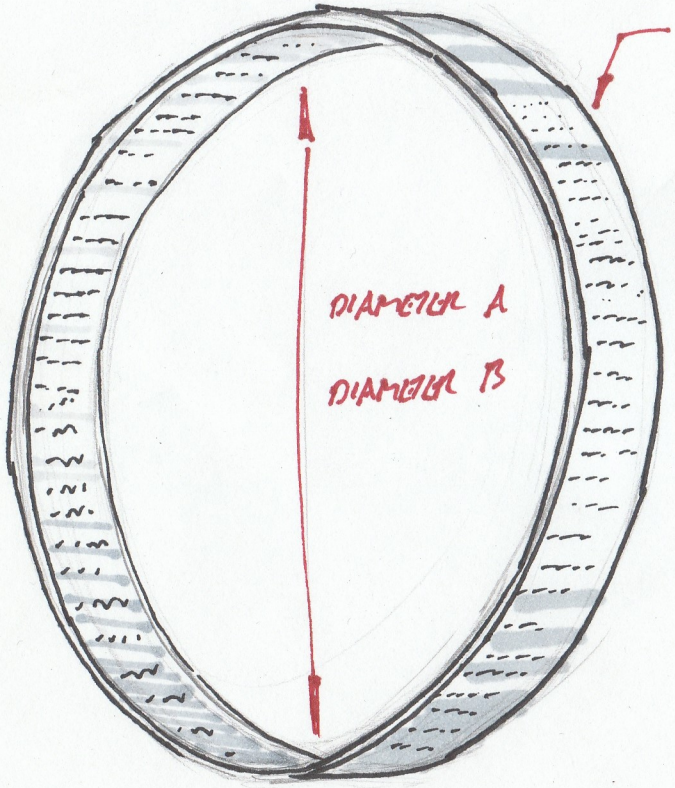

DIAMETER A
FOR LED AND PANAPLEX

$$\frac{60}{\text{MINUTES}} \times \frac{24}{\text{HOURS}} \times \frac{5}{\text{MM/MIN}} = \frac{7200}{\pi} = 2292 \text{ MM}$$

2292 MM OR 230 CM DIAMETER RING

DIAMETER B
FOR MIXIES

$$\frac{60}{\text{MINUTES}} \times \frac{12}{\text{HOURS}} \times \frac{5}{\text{MIN/MM}} = \frac{3600}{\pi} = 1146 \text{ MM}$$

1146 MM OR 114.6 CM RING

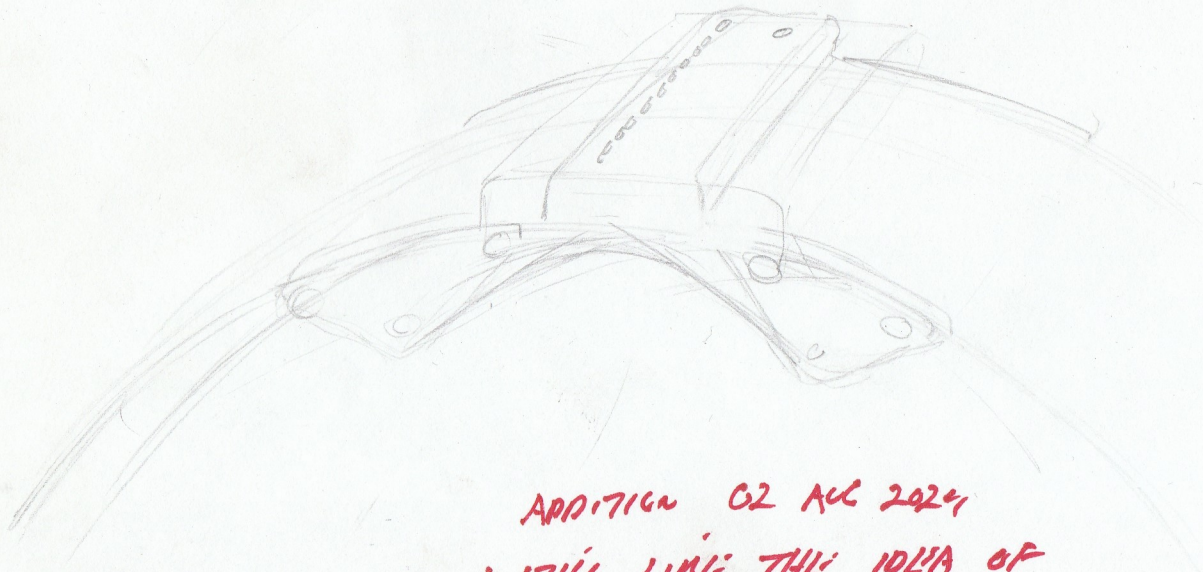

ADDITION 02 AUG 2024

I STILL LIKE THE IDEA OF
A 1 RPM MOTOR DRIVEN MICRO
SWITCH CLOCK
IT REPLACES THE JACQUARD LOOM
THE PUNCH CARDS.
IS THE ARTISTIC MERIT SUFFICIENT?
DOES IT OUTWEIGH THE TECHNICAL
EXERCISE?

ALAN

PROJECT DELAYED / ON HOLD

35
34.5

32.7
2.85